

Digital Clock Project Report

Mohit

March 24, 2025

Contents

1	Introduction	2
2	Hardware Components and Their Roles	2
2.1	ATmega328P (Arduino Uno)	2
2.2	SN7447 BCD-to-Seven-Segment Decoder/Driver	2
2.3	Seven-Segment Displays	2
2.4	Resistors	2
2.5	Push Buttons	2
3	Circuit Connections	3
3.1	Power and Ground	3
3.2	SN7447 Connections	3
3.3	Multiplexing and Digit Selection	3
3.4	Push Button Connections	4
4	Software Implementation and Code Explanation	4
4.1	Code Structure	4
4.1.1	Initialization	4
4.1.2	Multiplexing the Display	4
4.1.3	Timekeeping and Button Handling	5
4.2	Complete Code Listing	5
5	Conclusion	8

1 Introduction

This report describes the design and implementation of a digital clock using an ATmega328P microcontroller (the heart of an Arduino Uno), a SN7447 BCD-to-seven-segment decoder/-driver, and six common-anode seven-segment displays. Two push buttons allow the user to adjust the clock's hours and minutes. The design uses a multiplexing technique to drive all displays with a single SN7447 and directly controlled microcontroller outputs.

2 Hardware Components and Their Roles

2.1 ATmega328P (Arduino Uno)

The ATmega328P acts as the central controller for the clock. It:

- Generates 4-bit Binary Coded Decimal (BCD) signals to be sent to the SN7447.
- Controls which display is active via multiplexing.
- Reads the state of push buttons to adjust the time.

2.2 SN7447 BCD-to-Seven-Segment Decoder/Driver

The SN7447 decodes the 4-bit BCD input into the corresponding segment control signals for a seven-segment display. It is designed for common-anode displays, and its outputs are connected (via current-limiting resistors) in parallel to the segments of all six displays.

2.3 Seven-Segment Displays

Six common-anode seven-segment displays are used to show the time in HH:MM:SS format. Because only one SN7447 is used, the displays are multiplexed by sequentially activating each digit's common anode.

2.4 Resistors

- **Current-Limiting Resistors:** Each segment of every display is connected through a resistor (typically $220\text{--}330\Omega$) to limit the LED current.
- **Internal Pull-Up Resistors:** Enabled in software for the push buttons.

2.5 Push Buttons

Two push buttons are used:

- One for adjusting the hour.

- One for adjusting the minute.

They are wired between the microcontroller input pins and ground, utilizing the Arduino's internal pull-up resistors.

3 Circuit Connections

3.1 Power and Ground

- The Arduino's regulated 5V output powers the SN7447 and the displays.
- All ground lines (Arduino, SN7447, displays, and push buttons) are connected to a common ground.

3.2 SN7447 Connections

- **BCD Inputs:** Arduino digital pins 2, 3, 4, and 5 (mapped to PD2, PD3, PD4, and PD5 respectively) connect to the SN7447's BCD input pins.
- **Segment Outputs:** The outputs for segments *a* through *g* from the SN7447 are connected to all six seven-segment displays through individual current-limiting resistors.

3.3 Multiplexing and Digit Selection

Since only one SN7447 is used, the displays are multiplexed:

- Each display's common anode is directly connected to a microcontroller output pin.
- Pin assignments for digit selection are as follows:
 - Digit 1 (tens of hours): Arduino digital pin 6 (PD6)
 - Digit 2 (ones of hours): Arduino digital pin 7 (PD7)
 - Digit 3 (tens of minutes): Arduino digital pin 8 (PB0)
 - Digit 4 (ones of minutes): Arduino digital pin 9 (PB1)
 - Digit 5 (tens of seconds): Arduino digital pin 10 (PB2)
 - Digit 6 (ones of seconds): Arduino digital pin 11 (PB3)
- The microcontroller rapidly cycles through these outputs (multiplexing) so that all digits appear continuously lit.

3.4 Push Button Connections

- **Hour Adjust Button:** Connected between Arduino digital pin 12 (PB4) and ground, configured as an input with an internal pull-up.
- **Minute Adjust Button:** Connected between Arduino digital pin 13 (PB5) and ground, also configured with an internal pull-up.

4 Software Implementation and Code Explanation

The code is written in pure AVR C (using `avr-gcc`) and runs on the ATmega328P. It includes the following standard libraries:

- `<avr/io.h>`: Provides access to the microcontroller's registers (PORT, DDR, and PIN) for I/O operations.
- `<util/delay.h>`: Offers the `_delay_ms()` function for creating time delays necessary for multiplexing and debouncing.
- `<stdint.h>`: Supplies standard integer types (e.g., `uint8_t`) for portability.

4.1 Code Structure

4.1.1 Initialization

- **I/O Configuration:** The BCD output pins (PD2–PD5) are set as outputs. Digit select pins on PORTD (PD6, PD7) and PORTB (PB0–PB3) are also configured as outputs. The push button pins (PB4, PB5) are configured as inputs with enabled pull-ups.
- **Clock Variables:** Variables for hours, minutes, and seconds are initialized (default starting time: 12:00:00). A cycle counter is used to approximate a one-second interval based on the multiplexing delay.

4.1.2 Multiplexing the Display

- The current time is broken into six individual digits (HH:MM:SS).
- The code loops through each digit, sending the corresponding 4-bit BCD value to the SN7447 via PORTD (PD2–PD5).
- Only one display is activated at a time by setting the corresponding digit select pin HIGH.
- A short delay (e.g., 2ms) allows the digit to be visible before deactivating the display and moving to the next.
- Rapid cycling (multiplexing) creates the illusion that all six digits are lit simultaneously.

4.1.3 Timekeeping and Button Handling

- **Software Timekeeping:** A cycle counter increments with each complete multiplex cycle. When the counter reaches approximately 83 cycles (around 1 second), the seconds variable is incremented. When seconds, minutes, or hours reach their limits (60 or 24), the variables are reset and the next unit is incremented.
- **Push Button Adjustments:** The code polls the push button inputs. When a button is pressed (detected by a LOW signal), a debounce delay is introduced, and the corresponding time variable (hours or minutes) is incremented. The system waits until the button is released before continuing.

4.2 Complete Code Listing

```
1  /*
2  * Digital Clock using 6 seven-segment displays with SN7447 driver
3  * ATmega328P (Arduino Uno) version in pure C for avr-gcc
4  *
5  * Pin Mapping:
6  *   BCD outputs (to SN7447): Arduino pins 2-5  => PD2, PD3, PD4, PD5
7  *   Digit Select outputs:
8  *       Digit 1 (tens of hours): pin 6  => PD6
9  *       Digit 2 (ones of hours): pin 7  => PD7
10 *       Digit 3 (tens of minutes): pin 8  => PB0
11 *       Digit 4 (ones of minutes): pin 9  => PB1
12 *       Digit 5 (tens of seconds): pin 10 => PB2
13 *       Digit 6 (ones of seconds): pin 11 => PB3
14 *   Push Buttons:
15 *       Hour adjust: pin 12 => PB4 (input with pull-up)
16 *       Minute adjust: pin 13 => PB5 (input with pull-up)
17 */
18
19 #include <avr/io.h>
20 #include <util/delay.h>
21 #include <stdint.h>
22
23 #define DIGIT_DELAY_MS 2    // Delay per digit in milliseconds
24 #define NUM_DIGITS 6
25
26 int main(void) {
27     // I/O Setup
28     DDRD |= (1 << PD2) | (1 << PD3) | (1 << PD4) | (1 << PD5); // BCD
29     // Digit
30     DDRD |= (1 << PD6) | (1 << PD7);
31     // Digit
32     DDRB |= (1 << PB0) | (1 << PB1) | (1 << PB2) | (1 << PB3);
33     // Digit
34     // Configure push buttons on PB4 and PB5 as inputs with pull-ups
```

```

33 DDRB &= ~( (1 << PB4) | (1 << PB5));
34 PORTB |= (1 << PB4) | (1 << PB5);
35
36 // Initialize clock variables (12:00:00)
37 uint8_t hours = 12;
38 uint8_t minutes = 0;
39 uint8_t seconds = 0;
40 uint16_t cycle_count = 0; // For approximating a 1-second interval
41
42 while (1) {
43     // Break time into individual digits: HH:MM:SS
44     uint8_t digits[NUM_DIGITS];
45     digits[0] = hours / 10; // Tens of hours
46     digits[1] = hours % 10; // Ones of hours
47     digits[2] = minutes / 10; // Tens of minutes
48     digits[3] = minutes % 10; // Ones of minutes
49     digits[4] = seconds / 10; // Tens of seconds
50     digits[5] = seconds % 10; // Ones of seconds
51
52     // Multiplex through each digit
53     for (uint8_t i = 0; i < NUM_DIGITS; i++) {
54         // Set BCD outputs: Clear PD2-PD5 and set new value
55         PORTD = (PORTD & ~0x3C) | ((digits[i] << 2) & 0x3C);
56
57         // Activate corresponding digit
58         if (i < 2) {
59             if (i == 0)
60                 PORTD |= (1 << PD6); // Activate digit 1 (tens of
                                     // hours)
61             else
62                 PORTD |= (1 << PD7); // Activate digit 2 (ones of
                                     // hours)
63         } else {
64             PORTB |= (1 << (i - 2)); // Activate digits 3-6 (PB0-PB3)
65         }
66         _delay_ms(DIGIT_DELAY_MS); // Allow digit to be visible
67
68         // Deactivate digit
69         if (i < 2) {
70             if (i == 0)
71                 PORTD &= ~(1 << PD6);
72             else
73                 PORTD &= ~(1 << PD7);
74         } else {
75             PORTB &= ~(1 << (i - 2));
76         }
77     } // End multiplexing
78
79     cycle_count++;
80


```

```

81 // Check push buttons for time adjustment
82 if (!(PINB & (1 << PB4))) { // Hour adjustment button pressed
83     _delay_ms(50);
84     if (!(PINB & (1 << PB4))) {
85         hours = (hours + 1) % 24;
86         while (!(PINB & (1 << PB4)));
87         _delay_ms(50);
88     }
89 }
90 if (!(PINB & (1 << PB5))) { // Minute adjustment button pressed
91     _delay_ms(50);
92     if (!(PINB & (1 << PB5))) {
93         minutes = (minutes + 1) % 60;
94         while (!(PINB & (1 << PB5)));
95         _delay_ms(50);
96     }
97 }
98
99 // Update time approximately every 83 multiplex cycles (approx. 1
100 second)
101 if (cycle_count >= 83) {
102     cycle_count = 0;
103     seconds++;
104     if (seconds >= 60) {
105         seconds = 0;
106         minutes++;
107         if (minutes >= 60) {
108             minutes = 0;
109             hours++;
110             if (hours >= 24)
111                 hours = 0;
112         }
113     }
114 } // End main loop
115
116 return 0;
117 }

```

Listing 1: Digital Clock Code in AVR C

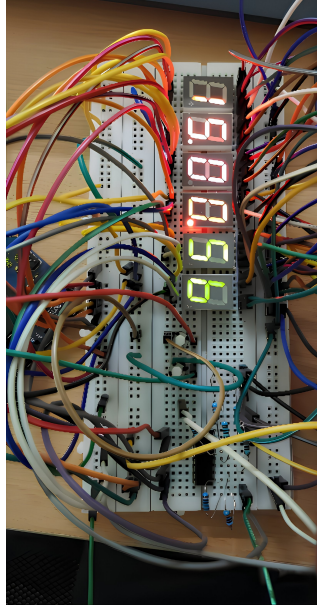

5 Conclusion

This project demonstrates how a digital clock can be implemented using minimal hardware by employing multiplexing techniques and a dedicated BCD-to-seven-segment decoder. The ATmega328P directly controls the SN7447 and the displays while handling timekeeping and user input via push buttons. The software, written in pure AVR C, efficiently manages the hardware through direct register manipulation and software delays. This report provides a comprehensive understanding of the hardware connections and the software architecture required to build and operate a digital clock.