# **Clock Project Report**

### EE224BTECH11044 - Muthyala koushik

### 1 Introduction

This project implements a digital clock using an Arduino Uno with a single SN7447 BCD-to-7-segment decoder. The clock displays hours, minutes, and seconds on six multiplexed 7-segment displays. Time is maintained in Binary Coded Decimal (BCD) format and updated every second using a Timer1 compare match interrupt.

### 2 Aim

- Design a digital clock that displays time in HH: MM: SS format.
- Use a single SN7447 decoder to drive six 7-segment displays through multiplexing.
- Update the time every second via an interrupt-driven timer.
- Implement BCD arithmetic to handle digit carry-overs across seconds, minutes, and hours.

# 3 Components Required

- Arduino Uno
- SN7447 BCD-to-7-segment decoder
- 6 common anode (or cathode, as required) 7-segment displays
- Current-limiting resistors (typically  $220 \Omega$  per segment)
- External 16 MHz clock source (or use the internal oscillator if applicable)
- Breadboard and connecting wires

# 4 Hardware Configuration

### 4.1 Pin Connections

The code defines two groups of connections:

a) **BCD Output to SN7447:** Four AVR pins provide the 4-bit Binary Coded Decimal (BCD) value to the SN7447.

SN7447 Input	Function	AVR Port/Pin	Digital Pin (Uno)
A (LSB)	BCD Data Bit 0	PD2	2
В	BCD Data Bit 1	PD3	3
С	BCD Data Bit 2	PD4	4
D (MSB)	BCD Data Bit 3	PD5	5

b) **Display Multiplex Control:** Six separate AVR pins are used to enable the common pin of each 7-segment display in a multiplexed arrangement.

Display Digit	Function	AVR Port/Pin	Digital Pin (Uno)
Hours Tens (H1)	Digit Enable Control	PD6	6
Hours Units (H2)	Digit Enable Control	PD7	7
Minutes Tens (M1)	Digit Enable Control	PB0	8
Minutes Units (M2)	Digit Enable Control	PB1	9
Seconds Tens (S1)	Digit Enable Control	PB2	10
Seconds Units (S2)	Digit Enable Control	PB3	11

### 4.2 Segment Wiring

- The outputs of the SN7447 decoder (segments a through g) are connected in parallel to the corresponding segments on all six 7-segment displays.
- Each segment connection should include a current-limiting resistor.
- The common pins of the displays (anode or cathode, depending on the type) are switched by the multiplex control lines.

### 4.3 Power Supply

Connection	Notes
VCC	+5V supply to SN7447, displays, and AVR
GND	Common ground for all components

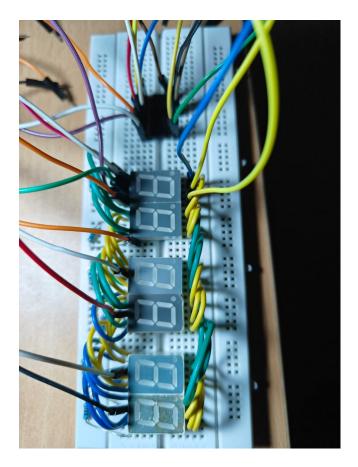


Figure 2: Block diagram of the digital clock system.

# 5 Software Design

### 5.1 Overall Architecture

The project firmware is divided into two main modules:

### a) Time Management:

- Time is stored in three volatile BCD variables: hours, minutes, and seconds.
- A Timer1 Compare Match interrupt (in CTC mode with a 1024 prescaler) updates the time every second.
- BCD arithmetic is used to increment seconds and handle carry-overs for minutes and hours.

### b) Display Multiplexing:

- The function displayTime() extracts individual digits from the BCD time values
- A single 4-bit BCD digit is sent to the SN7447 via the BCD output pins (PD2–PD5) using the function displayDigit().
- Each digit is displayed in sequence by enabling its corresponding control pin for a brief period (using \_delay\_ms()), creating the illusion of a continuously lit display.

### 5.2 Interrupt-Driven Time Update

- Timer1 is set to CTC mode with a prescaler of 1024, and the compare register is loaded with a value for a 1-second interval.
- The ISR (TIMER1\_COMPA\_vect) increments the seconds variable in BCD, performs digit carry operations, and updates minutes and hours accordingly.

### 6 Operation Workflow

### 1. Initialization:

- Configure BCD output pins (PD2–PD5) and display control pins (PD6, PD7, PB0–PB3) as outputs.
- Initialize Timer1 and enable global interrupts.

### 2. Time Update:

• Every second, the ISR updates the time variables using BCD arithmetic and carry management.

### 3. Display Refresh:

- The main loop continuously calls displayTime(), which sequentially enables each display digit.
- Each digit is shown for a short period, and rapid cycling creates persistenceof-vision.

# 7 Performance Specifications

• Voltage: 5V DC

• Clock Frequency: 16 MHz

• Time Update Accuracy: 1-second resolution (via Timer1 interrupt)

• Multiplexing Rate: Fast enough to achieve persistence-of-vision across 6 digits

## 8 Code Explanation

The following section explains the main parts of the digital clock code implemented on an Arduino Uno.

### 8.1 Preprocessor Directives and Includes

- #define F\_CPU 16000000UL: Sets the CPU clock frequency to 16 MHz. This definition is required by the delay routines from <util/delay.h>.
- #include <avr/io.h>: Includes the definitions for the input/output registers specific to the Arduino Uno.
- #include <avr/interrupt.h>: Provides the interrupt handling functions and macros
- #include <util/delay.h>: Enables the use of \_delay\_ms() for creating precise delays.

### 8.2 Pin Definitions and Hardware Connections

- BCD Pins (for SN7447 Decoder):
  - A is defined as PD2
  - B is defined as PD3
  - C is defined as PD4
  - D is defined as PD5

These pins send the 4-bit BCD value (representing a digit) to the SN7447 decoder.

### • Display Control Pins (for Multiplexing):

- Hours Tens (H1) is defined as PD6
- Hours Units (H2) is defined as PD7
- Minutes Tens (M1) is defined as PB0
- Minutes Units (M2) is defined as PB1
- Seconds Tens (S1) is defined as PB2
- Seconds Units (S2) is defined as PB3

These control pins are used to selectively enable each of the six 7-segment displays via multiplexing.

• Clock Variables: The variables hours, minutes, and seconds are declared as volatile uint8\_t and stored in BCD format. For example, hours is initialized to 0b00010010 (i.e., 12 in BCD).

### 8.3 Display Functions

- displayDigit(uint8\_t digit): This function sends a 4-bit BCD digit to the SN7447 decoder. It modifies PORTD by:
  - Clearing the bits corresponding to PD2–PD5 (using a bit mask).
  - Shifting the input digit into the correct bit positions.
- displayTime():
  - Extracts individual BCD digits for hours, minutes, and seconds.
  - For each digit (e.g., tens and units of hours, minutes, seconds), the function:
    - 1. Enables the appropriate display control pin.
    - 2. Calls displayDigit() to send the digit via the SN7447.

- 3. Uses \_delay\_ms() for a brief delay to ensure the digit is visible.
- 4. Disables the display control pin before moving to the next digit.
- This rapid cycling through digits (multiplexing) creates the illusion that all six displays are lit continuously.

### 8.4 Interrupt Service Routine (ISR)

- ISR(TIMER1\_COMPA\_vect): This routine is executed once per second, as determined by Timer1.
  - The seconds counter is incremented by one in BCD.
  - A series of conditional checks manage BCD carry:
    - \* When the lower nibble exceeds 9, it carries over by adding 0x10 (i.e., 16 in decimal) to the upper nibble.
    - \* If the seconds reach 60 (BCD value **0b01100000**), the seconds reset to 0 and minutes are incremented.
    - \* Similar checks apply for minutes and hours, with hours resetting after reaching 24 (BCD value 0b00100000).

### 8.5 Timer Initialization

- timer1\_init():
  - Configures Timer1 in CTC (Clear Timer on Compare) mode.
  - Sets the prescaler to 1024, which divides the 16 MHz clock.
  - Loads the Output Compare Register (OCR1A) with the value needed to achieve a 1-second interval.
  - Enables the Timer1 compare interrupt via TIMSK1.
  - Calls sei() to globally enable interrupts.

#### 8.6 Main Function

- main():
  - Configures the data direction registers:
    - \* DDRD is set for the BCD output pins (PD2–PD5) and the display control pins for hours (PD6 and PD7).
    - \* DDRB is set for the display control pins for minutes and seconds (PB0–PB3).
  - Calls timer1\_init() to initialize Timer1 and enable interrupts.
  - Enters an infinite loop in which displayTime() is continuously called.
    This ensures the display is refreshed rapidly to maintain the appearance of a continuously lit clock.